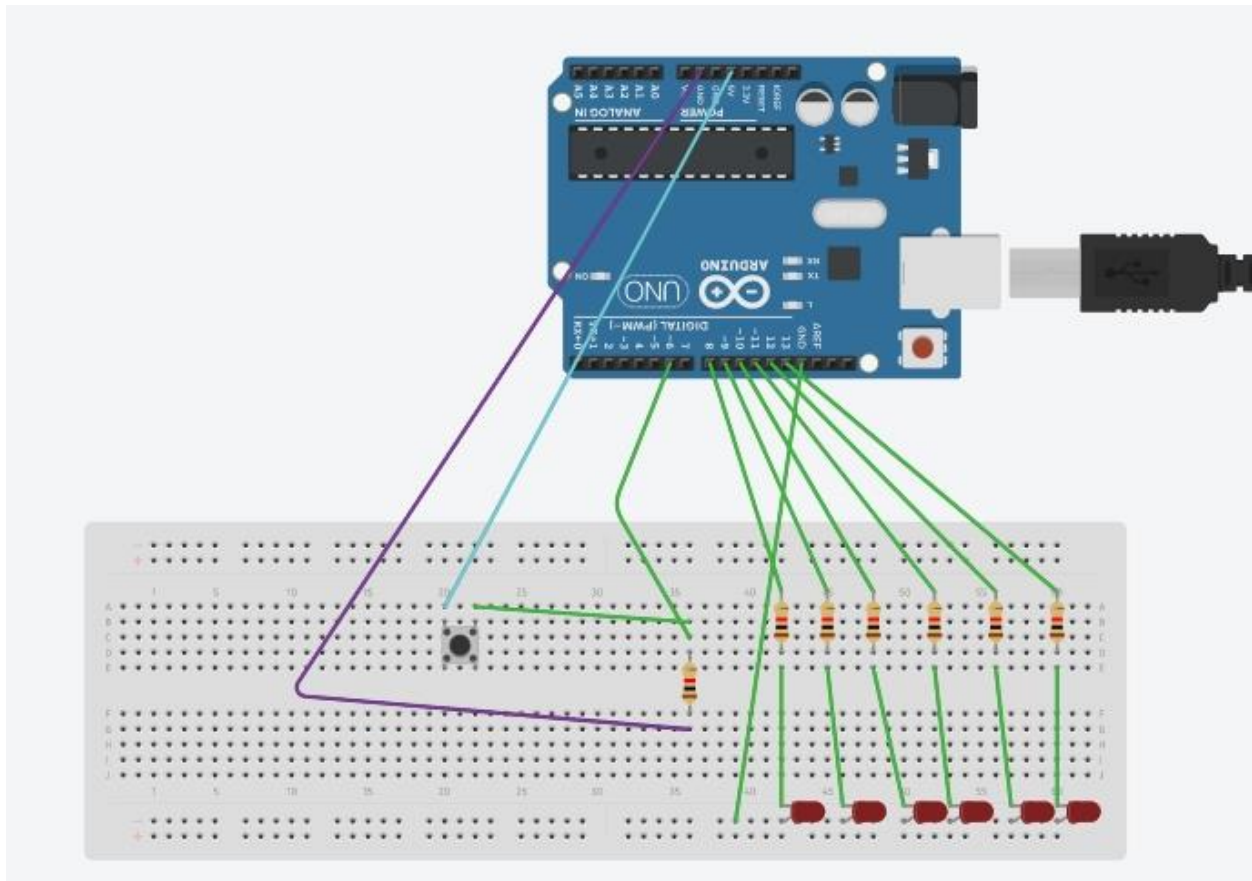


Aim: To design automatic led chaser (consisting of 6 led's)to generate two patterns which can be toggled with switch

A. pattern 1- led chaser

B. pattern 2- even, odd led's

Circuit diagram:



Hardware components:

1. **Arduino UNO ×1**
2. **5mm led ×6**
3. **Breadboard ×1**
4. **Jumper wires**
5. **Switch ×1**

Theory: In this experiment we have done coding to blink LED , which is held together on the breadboard.

Learning and Observations: The coding is done on computer from which the instructions are given to the Arduino Uno board . Arduino is a single board microcontroller meant to make the application more accessible which are interactive objects and its surroundings.

Procedure:

- *Take 6 led of different colours.*
- *Take one switch .*
- *Connect the cathode end of all led's to the GND pin of arduino.*
- *Connect the anode pin of all led's with each resistor connected to the end.*
- *Now connect the resistor ent to pins of arduino.*
- *And connect switch with circuit.*
- *Do all connections same as circuit diagram.*

Problems of trouble shooting:

1. *The incorrect coding might cause problems in the working of hardware .*
2. *Hardware should be correctly fitted on the breadboard or they might get fuse or damaged.*
3. *Arduino wire must be checked if they are losse or not and the ports should be properly cleaned before using they might cause problem in program.*

Precautions:

1. *The coding done on the software should be correct in every manner.All the errors should be avoided i.e. syntax logical errors etc.*
2. *All the wires and elements should be connected tightly and according to the coding done on system.*
3. *Positive and negative terminals should be put in correct order.*

Learning outcomes: from this experiment we have learn how to code in the software this project was the piller for the upcoming project .